

SY Div. C_ECA(2020 pattern) CIE test 3 on UNIT No. 05 and UNIT No 06-AY 2022-23 (Duration 1.30 Hrs)

Note: All the questions are mandatory. You can give this test only once and it can not be resubmitted. Solve all problems and upload the PDF or image of the solution. Write your name and Roll no. on each page.

aniket.22110125@viit.ac.in Switch account



Draft saved

The name, email, and photo associated with your Google account will be recorded when you upload files and submit this form

* Required

Select your division *

C



Enter your Complete GR number *

22110125

Enter your complete name *

Aniket Uday Supekar



Enter your complete Roll number *

213045

If V_{GS} is less than V_{th} , the E-MOSFET is working in -----region *

- ☒ cut off
- ☐ saturation
- ☐ Ohmic
- ☐ reverse saturation

MOSFET operates in saturation region has following parameters: $I_{DQ}=0.3 \text{ mA}$, $V_D=3 \text{ V}$, *
 $K=0.24 \text{ mA/V}^2$, $V_{tn}=1 \text{ V}$, Determine V_{GS} =-----

- ☐ 25.8
- ☐ 258 V
- ☐ 0.258 V
- ☒ 2.58 V

For CS MOSFET amplifier, the frequency of output signal is -----that of the input signal. *

- ☐ lower than
- ☐ equal to
- ☒ higher than



For N channel E-MOSFET having the parameters: $K_n = 1 \text{ mA/V}^2$, $V_{GS} = 0.99 \text{ V}$, $V_{tn} = 0.4 \text{ V}$. Determine I_{DQ} .

- ☐ 17.4 mA
- ☐ 0.0174 mA
- ☒ 0.174 mA
- ☐ 27.8 mA

Clear selection

For N channel E-MOSFET having the parameters: $\lambda = 0.02 \text{ V}^{-1}$, $I_{DQ} = 0.174 \text{ mA}$, Determine * small signal resistance (r_o) of the device.

- ☐ 0.28 Kohm
- ☐ 2.87 Kohm
- ☐ 100 Kohm
- ☒ 287 Kohm

For with bypass capacitor N ch. E-MOSFET CS amplifier, following parameters are given: * $V_{DD} = 5 \text{ V}$, $R_D = 7 \text{ Kohm}$, $V_{tn} = 0.8 \text{ V}$, $K_n = 2 \text{ mA/V}^2$, $I_{DQ} = 0.5 \text{ mA}$ and $\lambda = 0$. The values of g_m and A_v are respectively-----

- ☒ 1.41 mA/V, -9.87
- ☐ -1.41 mA/V, 9.87
- ☐ 7.45 mA/V, 15
- ☐ 7.45 mA/V, -15



Which of the following improvements is (are) a result of the negative feedback in a circuit? *

- ☐ Higher input impedance
- ☐ Better stabilized voltage gain
- ☐ Improved frequency response
- ☒ All of the above

Determine the voltage gain with feedback for a voltage-series feedback having $A = -100$, $R_I = 15 \text{ k}\Omega$, $R_o = 20 \text{ k}\Omega$, and a feedback of $\beta = -0.25$. *

- ☐ 3.85
- ☒ -3.85
- ☐ -9.09
- ☐ 9.09

Determine the input impedance with feedback for a voltage-series feedback having $A = -100$, $R_I = 15 \text{ k}\Omega$, $R_o = 20 \text{ k}\Omega$, and a feedback of $\beta = -0.25$. *

- ☐ 110 k Ω
- ☐ 290 k Ω
- ☒ 390 k Ω
- ☐ 510 k Ω



Voltage feedback connections tend to _____ the output impedance. Current feedback connections tend to _____ the output impedance. *

- ☒ decrease, increase
- ☐ increase, decrease
- ☐ increase, increase
- ☐ decrease, decrease
- ☐ Other:

If an amplifier has $A_v=100$, $BW=200$ KHz and $\beta=0.05$ then $BW_f=$ -----

- ☒ 1.2 MHz
- ☐ 12 MHz
- ☐ 0.12 MHz
- ☐ 120 MHz

Clear selection

9) In RC phase shift oscillator producing output at $f = 500$ Hz, $R = 7.5$ Kohm then $C =$ ----. *

- ☒ 0.01 micro F
- ☐ 0.017 micro F
- ☐ 0.012 nF
- ☐ 0.001 micro F



Upload solution as image or PDF (Max file size 10 MB) *



ECA CIE - 3 , (21... X



Send me a copy of my responses.

Page 1 of 1

Submit

Clear form

Never submit passwords through Google Forms.

This form was created inside of Vishwakarma Institute of Information Technology. [Report Abuse](#)

Google Forms



